

COE 200, Term 042

Fundamentals of Computer Engineering

HW# 8

- Q.1.** Using minimum number of gates and Full-Adders design a circuit that multiplies an 8-bit number X by 10.

Hint: $10*X = 8*X + 2*X$

- Q.2.** Implement a 4-to-16 Decoder using the minimum number of 2-to-4 decoders with enable inputs. If the resulting 4-to-16 Decoder is to be provided with an enable input En, show the modified circuit.

- Q.3.** Implement the following functions using minimum-sized Decoders and minimum number of extra gates:

a. $F(X,Y,Z) = XY + Z$

b. $F(A,B,C,D) = D(A' + B)$

c. $F(X,Y,Z) = X'(Y' + Z') + YZ'$

d. $F(X,Y,Z) = X'(Y' + Z') + XZ$

e. $F(A,B,C) = A'$

f. $F(A,B,C,D,E) = 1$

g. $F(A,B,C,D,E,G,H) = 0$

h. $F(X,Y,Z) = \sum(0,3,5,6)$, $d(X,Y,Z) = \sum(1,2,4,7)$

i. $F(A,B,C,D) = \prod(1,7,9,13,15)$

- Q.4.** Construct a 5-to-32 line decoder with four 3-to-8 line decoders with enable input and one 2-to-4 line decoder.

- Q.5.** A Combinational circuit is defined by the following three Boolean functions:

$$F_1(X, Y, Z) = X'Y' + XYZ'$$

$$F_2(X, Y, Z) = X' + Z$$

$$F_3(X, Y, Z) = XY + X'Y'$$

Design the circuit with a 3x8 decoder, four 2-input OR gates, and an inverter.