

Integer Multiplication and Division

COE 308

Computer Architecture

Prof. Muhamed Mudawar

Computer Engineering Department

King Fahd University of Petroleum and Minerals

Presentation Outline

- ❖ Unsigned Multiplication
- ❖ Signed Multiplication
- ❖ Faster Multiplication
- ❖ Unsigned Division
- ❖ Signed Division
- ❖ Multiplication and Division in MIPS

Unsigned Multiplication

❖ Paper and Pencil Example:



$$\begin{array}{r}
 \text{Multiplicand} \quad 1100_2 = 12 \\
 \text{Multiplier} \quad \times 1101_2 = 13 \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 1100 \\
 \hline
 \text{Product} \quad 10011100_2 = 156
 \end{array}$$

Binary multiplication is easy
 $0 \times \text{multiplicand} = 0$
 $1 \times \text{multiplicand} = \text{multiplicand}$

- ❖ m -bit multiplicand \times n -bit multiplier = $(m+n)$ -bit product
- ❖ Accomplished via **shifting** and **addition**
- ❖ Consumes more time and more chip area

Version 1 of Multiplication Hardware

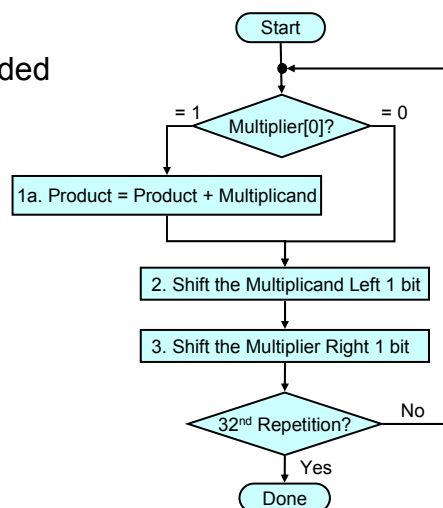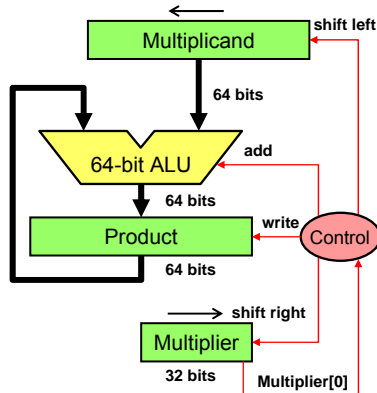- ❖ Initialize Product = 0
- ❖ Multiplicand is zero extended



Multiplication Example (Version 1)

- ❖ Consider: $1100_2 \times 1101_2$, Product = 10011100_2
- ❖ 4-bit multiplicand and multiplier are used in this example
- ❖ Multiplicand is zero extended because it is **unsigned**

Iteration		Multiplicand	Multiplier	Product
0	Initialize	00001100	1101	00000000
1	Multiplier[0] = 1 => ADD			+→ 00001100
	SLL Multiplicand and SRL Multiplier	00011000	0110	
2	Multiplier[0] = 0 => Do Nothing			00001100
	SLL Multiplicand and SRL Multiplier	00110000	0011	
3	Multiplier[0] = 1 => ADD			+→ 00111100
	SLL Multiplicand and SRL Multiplier	01100000	0001	
4	Multiplier[0] = 1 => ADD			+→ 10011100
	SLL Multiplicand and SRL Multiplier	11000000	0000	

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 5

Observation on Version 1 of Multiply

- ❖ Hardware in version 1 can be optimized
- ❖ Rather than shifting the multiplicand to the left
Instead, **shift the product to the right**
Has the same net effect and produces the same results
- ❖ Reduce Hardware
 - ✧ Multiplicand register can be reduced to 32 bits only
 - ✧ We can also reduce the adder size to 32 bits
- ❖ One cycle per iteration
 - ✧ Shifting and addition can be done simultaneously


Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 6

Version 2 of Multiplication Hardware

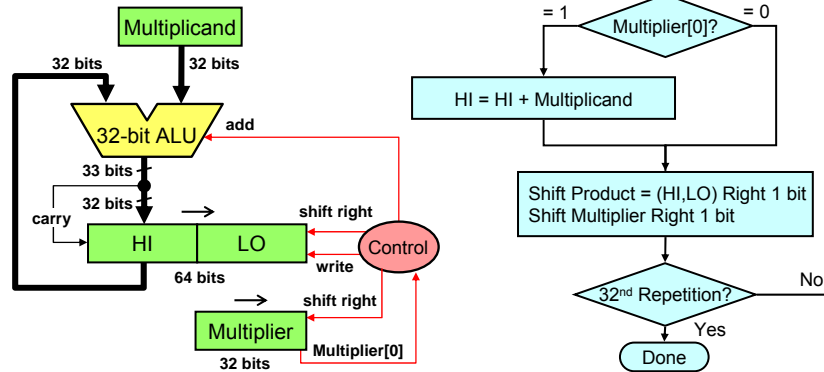- ❖ Product = HI and LO registers
- ❖ Product is shifted right
- ❖ Reduced 32-bit Multiplicand & Adder




Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 7

Refined Version of Multiply Hardware

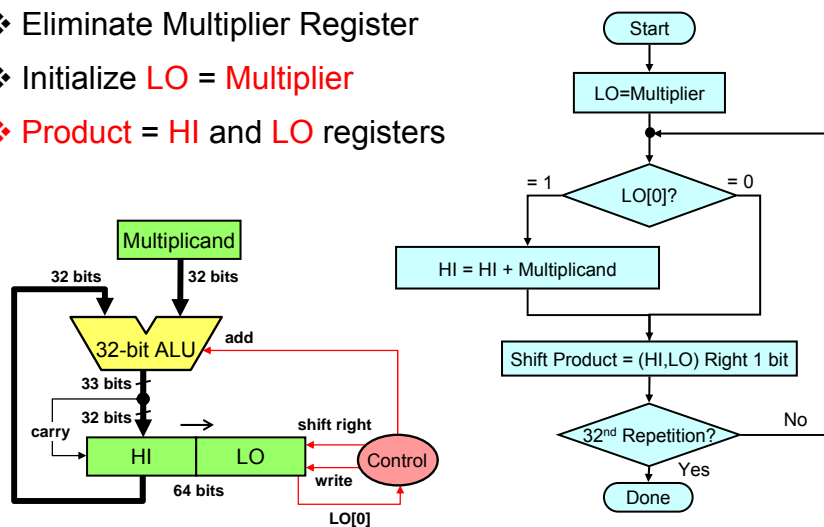- ❖ Eliminate Multiplier Register
- ❖ Initialize LO = Multiplier
- ❖ Product = HI and LO registers



Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 8

Multiply Example (Refined Version)

- ❖ Consider: $1100_2 \times 1101_2$, Product = 10011100_2
- ❖ 4-bit multiplicand and multiplier are used in this example
- ❖ 4-bit adder produces a **5-bit sum** (with carry)

Iteration		Multiplicand	Carry	Product = HI, LO
0	Initialize (LO = Multiplier)	1 1 0 0		0 0 0 0 1 1 0 1
1	LO[0] = 1 => ADD	1 1 0 0	0	1 1 0 0 1 1 0 1
	Shift Right Product = (HI, LO)	1 1 0 0		0 1 1 0 0 1 1 0
2	LO[0] = 0 => Do Nothing			
	Shift Right Product = (HI, LO)	1 1 0 0		0 0 1 1 0 0 1 1
3	LO[0] = 1 => ADD	1 1 0 0	0	1 1 1 1 0 0 1 1
	Shift Right Product = (HI, LO)	1 1 0 0		0 1 1 1 1 0 0 1
4	LO[0] = 1 => ADD	1 1 0 0	1	0 0 1 1 1 0 0 1
	Shift Right Product = (HI, LO)	1 1 0 0		1 0 0 1 1 1 0 0

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 9

Next ...

- ❖ Unsigned Multiplication
- ❖ **Signed Multiplication**
- ❖ Faster Multiplication
- ❖ Unsigned Division
- ❖ Signed Division
- ❖ Multiplication and Division in MIPS

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 10

Signed Multiplication

- ❖ So far, we have dealt with unsigned integer multiplication
- ❖ Version 1 of Signed Multiplication
 - ✧ Convert multiplier and multiplicand into positive numbers
 - If negative then obtain the 2's complement and remember the sign
 - ✧ Perform unsigned multiplication
 - ✧ Compute the sign of the product
 - ✧ If product sign < 0 then obtain the 2's complement of the product
- ❖ Refined Version:
 - ✧ Use the refined version of the unsigned multiplication hardware
 - ✧ When shifting right, **extend the sign** of the product
 - ✧ If multiplier is negative, the **last step** should be a **subtract**

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 11

Signed Multiplication (Pencil & Paper)

❖ Case 1: Positive Multiplier

$$\begin{array}{r} \text{Multiplicand} \quad 1100_2 = -4 \\ \text{Multiplier} \quad \times \quad 0101_2 = +5 \\ \hline \end{array}$$

$$\text{Sign-extension} \left\{ \begin{array}{l} \rightarrow 11111100 \\ \rightarrow 111100 \end{array} \right.$$

$$\text{Product} \quad 11101100_2 = -20$$

❖ Case 2: Negative Multiplier

$$\begin{array}{r} \text{Multiplicand} \quad 1100_2 = -4 \\ \text{Multiplier} \quad \times \quad 1101_2 = -3 \\ \hline \end{array}$$

$$\text{Sign-extension} \left\{ \begin{array}{l} \rightarrow 11111100 \\ \rightarrow 111100 \\ 00100 \quad (\text{2's complement of } 1100) \end{array} \right.$$

$$\text{Product} \quad 00001100_2 = +12$$

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 12



Signed Multiplication Hardware

❖ Similar to Unsigned Multiplier

❖ ALU produces a **33-bit** result

❖ Multiplicand and HI are **sign-extended**

❖ **Sign** is the sign of the result

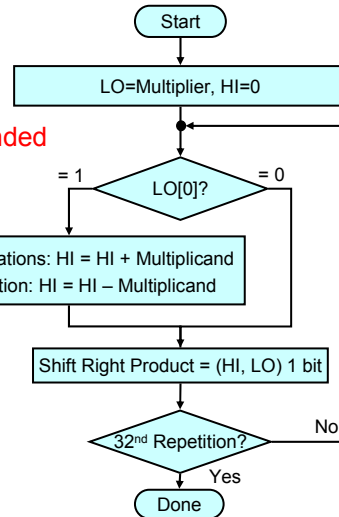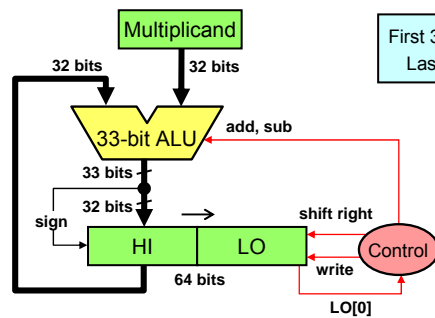

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 13

Signed Multiplication Example

❖ Consider: $1100_2 (-4) \times 1101_2 (-3)$, Product = 00001100_2

❖ Multiplicand and HI are **sign-extended** before addition

❖ Last iteration: add 2's complement of Multiplicand

Iteration		Multiplicand	Sign	Product = HI, LO
0	Initialize (LO = Multiplier)	1 1 0 0		0 0 0 0 1 1 0 1
1	LO[0] = 1 => ADD	1 1 0 0	1	1 1 0 0 1 1 0 1
	Shift Product = (HI, LO) right 1 bit	1 1 0 0		1 1 1 0 0 1 1 0
2	LO[0] = 0 => Do Nothing			
	Shift Product = (HI, LO) right 1 bit	1 1 0 0		1 1 1 1 0 0 1 1
3	LO[0] = 1 => ADD	1 1 0 0	1	1 0 1 1 0 0 1 1
	Shift Product = (HI, LO) right 1 bit	1 1 0 0		1 1 0 1 1 0 0 1
4	LO[0] = 1 => SUB (ADD 2's compl)	0 1 0 0	0	0 0 0 1 1 0 0 1
	Shift Product = (HI, LO) right 1 bit			0 0 0 0 1 1 0 0

Integer Multiplication and Division

COE 308 – Computer Architecture


© Muhamed Mudawar – slide 14

Next ...

- ❖ Unsigned Multiplication
- ❖ Signed Multiplication
- ❖ **Faster Multiplication**
- ❖ Unsigned Division
- ❖ Signed Division
- ❖ Multiplication and Division in MIPS


Faster Multiplication Hardware

- ❖ 32-bit adder for each bit of the multiplier
 - ❖ 31 adders are needed for a 32-bit multiplier
 - ❖ AND multiplicand with each bit of multiplier
 - ❖ Product = accumulated shifted sum
- ❖ Each adder produces a 33-bit output
 - ❖ Most significant bit is a carry bit
 - ❖ Least significant bit is a product bit
 - ❖ Upper 32 bits go to next adder
- ❖ Array multiplier can be optimized
 - ❖ Carry save adders reduce delays
 - ❖ Pipelining further improves the speed

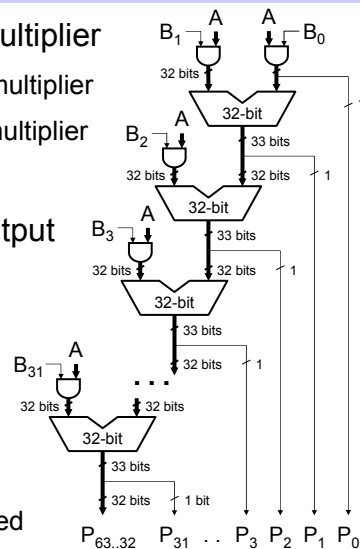

Carry Save Adders

 - ❖ Used when adding multiple numbers (as in multipliers)
- ❖ All the bits of a carry save adder work in parallel
 - ❖ The carry does not propagate as in a ripple-carry adder
 - ❖ This is why the carry save adder is much faster than ripple-carry
- ❖ A carry save adder has 3 inputs and produces two outputs
 - ❖ It adds 3 numbers and produces partial sum and carry bits




Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 17

Consider Adding: $S = A + B + C + D$

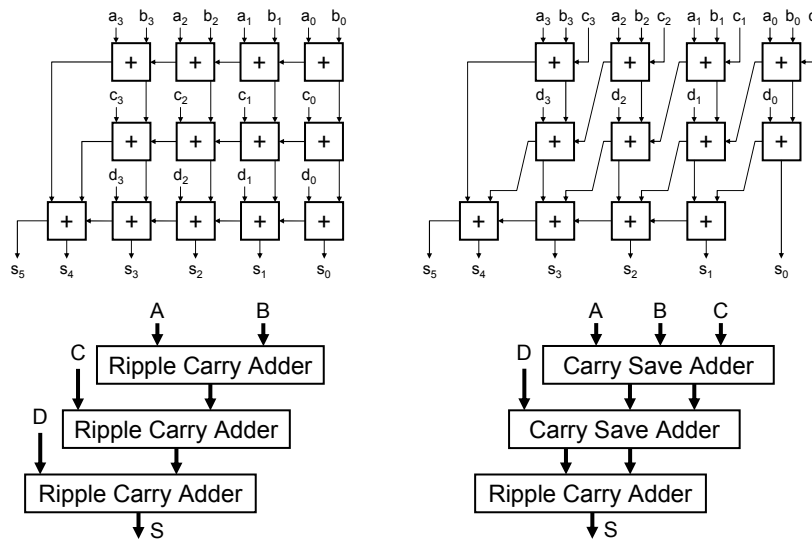

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 18

Next ...

- ❖ Unsigned Multiplication
- ❖ Signed Multiplication
- ❖ Faster Multiplication
- ❖ **Unsigned Division**
- ❖ Signed Division
- ❖ Multiplication and Division in MIPS

Unsigned Division (Paper & Pencil)

$$\begin{array}{r}
 \text{Divisor } 1011_2 \) \ 11011001_2 \\
 \underline{-1011} \\
 10 \\
 \underline{101} \\
 1010 \\
 \underline{10100} \\
 -1011 \\
 \underline{1001} \\
 10011 \\
 \underline{-1011} \\
 1000_2
 \end{array}$$

$10011_2 = 19$ **Quotient**
 $11011001_2 = 217$ **Dividend**

 $1000_2 = 8$ **Remainder**

Dividend =
 Quotient × Divisor
 + Remainder
 $217 = 19 \times 11 + 8$



Try to see how big a number can be subtracted, creating a digit of the quotient on each attempt

Binary division is accomplished via shifting and subtraction

First Division Algorithm & Hardware

❖ Initialize:

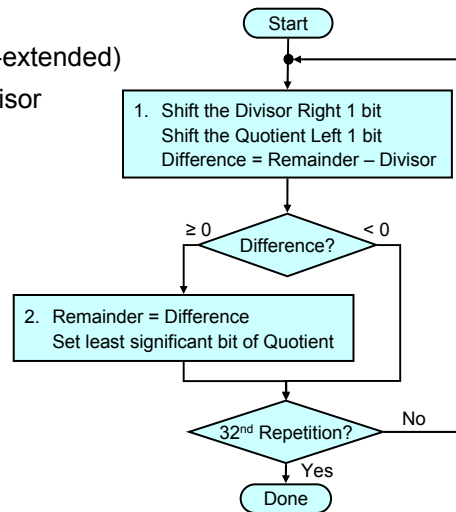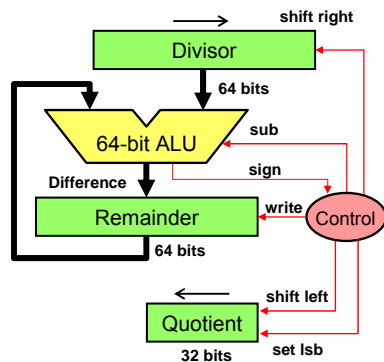- ❖ Remainder = Dividend (0-extended)
- ❖ Load Upper 32 bits of Divisor
- ❖ Quotient = 0



Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 21

Division Example (Version 1)

- ❖ Consider: $1110_2 / 0011_2$ (4-bit dividend & divisor)
- ❖ Quotient = 0100_2 and Remainder = 0010_2
- ❖ 8-bit registers for Remainder and Divisor (8-bit ALU)

Iteration		Remainder	Divisor	Difference	Quotient
0	Initialize	0000 1110	0011 0000		0000
1	1: SRL Div, SLL Q, Difference	00001110	00011000	11110110	0000
	2: Diff < 0 => Do Nothing				
2	1: SRL Div, SLL Q, Difference	00001110	00001100	00000010	0000
	2: Rem = Diff, set lsb Quotient	00000010			000 1
3	1: SRL Div, SLL Q, Difference	00000010	00000110	11111100	0010
	2: Diff < 0 => Do Nothing				
4	1: SRL Div, SLL Q, Difference	00000010	00000011	11111111	0100
	2: Diff < 0 => Do Nothing				

Integer Multiplication and Division

COE 308 – Computer Architecture



© Muhamed Mudawar – slide 22

Observations on Version 1 of Divide

- ❖ Version 1 of Division hardware can be optimized
- ❖ Instead of shifting divisor right,
 - Shift the remainder register left
 - Has the same net effect and produces the same results
- ❖ Reduce Hardware:
 - ❖ Divisor register can be reduced to 32 bits (instead of 64 bits)
 - ❖ ALU can be reduced to 32 bits (instead of 64 bits)
 - ❖ Remainder and Quotient registers can be combined

Refined Division Hardware

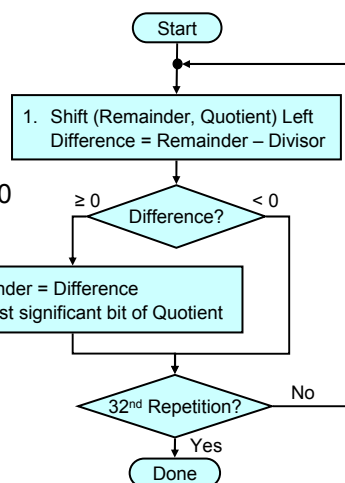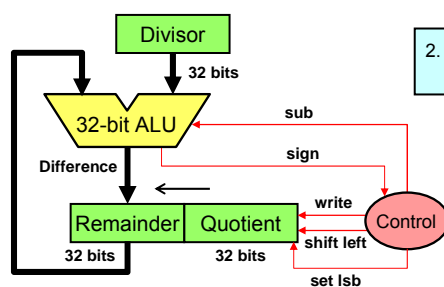- ❖ Observation:
 - ❖ Shifting remainder left does the same as shifting the divisor right
- ❖ Initialize:
 - ❖ Quotient = Dividend, Remainder = 0



Division Example (Refined Version)

- ❖ Same Example: $1110_2 / 0011_2$ (4-bit dividend & divisor)
- ❖ Quotient = 0100_2 and Remainder = 0010_2
- ❖ 4-bit registers for Remainder and Divisor (4-bit ALU)

Iteration		Remainder	Quotient	Divisor	Difference
0	Initialize	0 0 0 0	1 1 1 0	0 0 1 1	
1	1: Shift Left, Difference	0 0 0 1 ←	1 1 0 0	0 0 1 1	1 1 1 0
	2: Diff < 0 => Do Nothing				
2	1: Shift Left, Difference	0 0 1 1 ←	1 0 0 0	0 0 1 1	0 0 0 0
	2: Rem = Diff, set lsb Quotient	0 0 0 0	1 0 0 1		
3	1: Shift Left, Difference	0 0 0 1 ←	0 0 1 0	0 0 1 1	1 1 1 0
	2: Diff < 0 => Do Nothing				
4	1: Shift Left, Difference	0 0 1 0 ←	0 1 0 0	0 0 1 1	1 1 1 1
	2: Diff < 0 => Do Nothing				

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 25

Next ...

- ❖ Unsigned Multiplication
- ❖ Signed Multiplication
- ❖ Faster Multiplication
- ❖ Unsigned Division
- ❖ Signed Division
- ❖ Multiplication and Division in MIPS

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 26

Signed Division

- ❖ Simplest way is to remember the signs
- ❖ Convert the dividend and divisor to positive
 - ❖ Obtain the 2's complement if they are negative
- ❖ Do the unsigned division
- ❖ Compute the signs of the quotient and remainder
 - ❖ Quotient sign = Dividend sign XOR Divisor sign
 - ❖ Remainder sign = Dividend sign
- ❖ Negate the quotient and remainder if their sign is negative
 - ❖ Obtain the 2's complement to convert them to negative

Signed Division Examples

1. **Positive** Dividend and **Positive** Divisor
 - ❖ Example: $+17 / +3$ Quotient = +5 Remainder = +2
2. **Positive** Dividend and **Negative** Divisor
 - ❖ Example: $+17 / -3$ Quotient = -5 Remainder = +2
3. **Negative** Dividend and **Positive** Divisor
 - ❖ Example: $-17 / +3$ Quotient = -5 Remainder = -2
4. **Negative** Dividend and **Negative** Divisor
 - ❖ Example: $-17 / -3$ Quotient = +5 Remainder = -2

The following equation must always hold:


$$\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$$

Next ...

- ❖ Unsigned Multiplication
- ❖ Signed Multiplication
- ❖ Faster Multiplication
- ❖ Unsigned Division
- ❖ Signed Division
- ❖ **Multiplication and Division in MIPS**


Multiplication in MIPS

- ❖ Two Multiply instructions
 - ❖ `mult $s1,$s2` **Signed multiplication**
 - ❖ `multu $s1,$s2` **Unsigned multiplication**
- ❖ 32-bit multiplication produces a 64-bit Product
- ❖ Separate pair of 32-bit registers
 - ❖ **HI = high-order 32-bit**
 - ❖ **LO = low-order 32-bit**
 - ❖ Result of multiplication is always in HI & LO
- ❖ Moving data from HI/LO to MIPS registers
 - ❖ `mfhi Rd` (move from HI to Rd)
 - ❖ `mflo Rd` (move from LO to Rd)

 

Division in MIPS

- ❖ Two Divide instructions
 - ✧ `div $s1,$s2` **Signed division**
 - ✧ `divu $s1,$s2` **Unsigned division**
- ❖ Division produces quotient and remainder
- ❖ Separate pair of 32-bit registers
 - ✧ **HI = 32-bit remainder**
 - ✧ **LO = 32-bit quotient**
 - ✧ If divisor is 0 then result is **unpredictable**
- ❖ Moving data to HI/LO from MIPS registers
 - ✧ `mthi Rs` (move to HI from Rs)
 - ✧ `mtlo Rs` (move to LO from Rs)

 

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 31

Integer Multiply/Divide Instructions

Instruction	Meaning	Format						
<code>mult Rs, Rt</code>	Hi, Lo = $R_s \times R_t$	$op^6 = 0$	R_s^5	R_t^5	0	0	0x18	
<code>multu Rs, Rt</code>	Hi, Lo = $R_s \times R_t$	$op^6 = 0$	R_s^5	R_t^5	0	0	0x19	
<code>div Rs, Rt</code>	Hi, Lo = R_s / R_t	$op^6 = 0$	R_s^5	R_t^5	0	0	0x1a	
<code>divu Rs, Rt</code>	Hi, Lo = R_s / R_t	$op^6 = 0$	R_s^5	R_t^5	0	0	0x1b	
<code>mfhi Rd</code>	$R_d = Hi$	$op^6 = 0$	0	0	R_d^5	0	0x10	
<code>mflo Rd</code>	$R_d = Lo$	$op^6 = 0$	0	0	R_d^5	0	0x12	
<code>mthi Rs</code>	$Hi = R_s$	$op^6 = 0$	R_s^5	0	0	0	0x11	
<code>mtlo Rs</code>	$Lo = R_s$	$op^6 = 0$	R_s^5	0	0	0	0x13	

- ❖ Signed arithmetic: `mult`, `div` (R_s and R_t are signed)
 - ✧ LO = 32-bit low-order and HI = 32-bit high-order of multiplication
 - ✧ LO = 32-bit quotient and HI = 32-bit remainder of division
- ❖ Unsigned arithmetic: `multu`, `divu` (R_s and R_t are unsigned)
- ❖ **NO arithmetic exception** can occur

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 32

Integer to String Conversion

- ❖ Objective: convert an unsigned 32-bit integer to a string
- ❖ How to obtain the decimal digits of the number?
 - ◇ Divide the number by 10, Remainder = decimal digit (0 to 9)
 - ◇ Convert decimal digit into its ASCII representation ('0' to '9')
 - ◇ Repeat the division until the quotient becomes zero
 - ◇ Digits are computed **backwards** from least to most significant
- ❖ Example: convert 2037 to a string
 - ◇ Divide 2037/10 quotient = 203 remainder = 7 char = '7'
 - ◇ Divide 203/10 quotient = 20 remainder = 3 char = '3'
 - ◇ Divide 20/10 quotient = 2 remainder = 0 char = '0'
 - ◇ Divide 2/10 quotient = 0 remainder = 2 char = '2'

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 33

Integer to String Procedure

```
#-----  
# int2str:    Converts an unsigned integer into a string  
# Parameters: $a0 = integer to be converted  
#            $a1 = string pointer (can store 10 digits)  
#-----  
int2str:  
    move    $t0, $a0            # $t0 = dividend = integer value  
    li      $t1, 10            # $t1 = divisor = 10  
    addiu   $a1, $a1, 10       # start at end of string  
    sb      $zero, 0($a1)      # store a NULL byte  
convert:  
    divu    $t0, $t1           # LO = quotient, HI = remainder  
    mflo    $t0                # $t0 = quotient  
    mfhi    $t2                # $t2 = remainder  
    ori     $t2, $t2, 0x30     # convert digit to a character  
    addiu   $a1, $a1, -1       # point to previous char  
    sb      $t2, 0($a1)       # store digit character  
    bnez    $t0, convert       # loop if quotient is not 0  
    jr      $ra
```

Integer Multiplication and Division

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 34