

Single Cycle Processor Design

COE 308

Computer Architecture

Prof. Muhamed Mudawar

Computer Engineering Department

King Fahd University of Petroleum and Minerals


Presentation Outline

- ❖ **Designing a Processor: Step-by-Step**
- ❖ Datapath Components and Clocking
- ❖ Assembling an Adequate Datapath
- ❖ Controlling the Execution of Instructions
- ❖ The Main Controller and ALU Controller
- ❖ Drawback of the single-cycle processor design

The Performance Perspective

❖ Recall, performance is determined by:

 - ❖ Instruction count
- ❖ Clock cycles per instruction (CPI)
- ❖ Clock cycle time



❖ Processor design will affect

- ❖ Clock cycles per instruction
- ❖ Clock cycle time

❖ Single cycle datapath and control design:

- ❖ Advantage: One clock cycle per instruction
- ❖ Disadvantage: long cycle time

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 3

Designing a Processor: Step-by-Step

❖ Analyze instruction set => **datapath requirements**

- ❖ The meaning of each instruction is given by the **register transfers**
- ❖ Datapath must include storage elements for ISA registers
- ❖ Datapath must support each register transfer

❖ Select **datapath components** and **clocking methodology**

❖ Assemble **datapath** meeting the requirements

❖ Analyze implementation of **each instruction**

- ❖ Determine the setting of **control signals** for register transfer

❖ Assemble the **control logic**


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 4

Review of MIPS Instruction Formats

 - ❖ All instructions are **32-bit wide**
- ❖ Three instruction formats: **R-type**, **I-type**, and **J-type**



- ❖ Op⁶: 6-bit opcode of the instruction
- ❖ Rs⁵, Rt⁵, Rd⁵: 5-bit source and destination register numbers
- ❖ sa⁵: 5-bit shift amount used by shift instructions
- ❖ funct⁶: 6-bit function field for R-type instructions
- ❖ immediate¹⁶: 16-bit immediate value or address offset
- ❖ immediate²⁶: 26-bit target address of the jump instruction

MIPS Subset of Instructions

- ❖ Only a subset of the MIPS instructions are considered
 - ❖ ALU instructions (R-type): **add, sub, and, or, xor, slt**
 - ❖ Immediate instructions (I-type): **addi, slti, andi, ori, xori**
 - ❖ Load and Store (I-type): **lw, sw**
 - ❖ Branch (I-type): **beq, bne**
 - ❖ Jump (J-type): **j**
- ❖ This subset does not include all the integer instructions
- ❖ But sufficient to illustrate design of datapath and control
- ❖ Concepts used to implement the MIPS subset are used to construct a broad spectrum of computers

Details of the MIPS Subset

Instruction	Meaning	Format						
add rd, rs, rt	addition	op ⁶ = 0	rs ⁵	rt ⁵	rd ⁵	0	0x20	
sub rd, rs, rt	subtraction	op ⁶ = 0	rs ⁵	rt ⁵	rd ⁵	0	0x22	
and rd, rs, rt	bitwise and	op ⁶ = 0	rs ⁵	rt ⁵	rd ⁵	0	0x24	
or rd, rs, rt	bitwise or	op ⁶ = 0	rs ⁵	rt ⁵	rd ⁵	0	0x25	
xor rd, rs, rt	exclusive or	op ⁶ = 0	rs ⁵	rt ⁵	rd ⁵	0	0x26	
slt rd, rs, rt	set on less than	op ⁶ = 0	rs ⁵	rt ⁵	rd ⁵	0	0x2a	
addi rt, rs, im ¹⁶	add immediate	0x08	rs ⁵	rt ⁵	im ¹⁶			
slti rt, rs, im ¹⁶	slt immediate	0x0a	rs ⁵	rt ⁵	im ¹⁶			
andi rt, rs, im ¹⁶	and immediate	0x0c	rs ⁵	rt ⁵	im ¹⁶			
ori rt, rs, im ¹⁶	or immediate	0x0d	rs ⁵	rt ⁵	im ¹⁶			
xori rt, im ¹⁶	xor immediate	0x0e	rs ⁵	rt ⁵	im ¹⁶			
lw rt, im ¹⁶ (rs)	load word	0x23	rs ⁵	rt ⁵	im ¹⁶			
sw rt, im ¹⁶ (rs)	store word	0x2b	rs ⁵	rt ⁵	im ¹⁶			
beq rs, rt, im ¹⁶	branch if equal	0x04	rs ⁵	rt ⁵	im ¹⁶			
bne rs, rt, im ¹⁶	branch not equal	0x05	rs ⁵	rt ⁵	im ¹⁶			
j im ²⁶	jump	0x02	im ²⁶					

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 7

Register Transfer Level (RTL)

- ❖ RTL is a description of data flow between registers
- ❖ RTL gives a **meaning** to the instructions
- ❖ All instructions are fetched from memory at address PC

Instruction RTL Description

ADD	Reg(Rd) ← Reg(Rs) + Reg(Rt);	PC ← PC + 4
SUB	Reg(Rd) ← Reg(Rs) – Reg(Rt);	PC ← PC + 4
ORI	Reg(Rt) ← Reg(Rs) zero_ext(1m16);	PC ← PC + 4
LW	Reg(Rt) ← MEM[Reg(Rs) + sign_ext(1m16)];	PC ← PC + 4
SW	MEM[Reg(Rs) + sign_ext(1m16)] ← Reg(Rt);	PC ← PC + 4
BEQ	if (Reg(Rs) == Reg(Rt)) PC ← PC + 4 + 4 × sign_extend(1m16) else PC ← PC + 4	

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 8

Instructions are Executed in Steps

❖ R-type	Fetch instruction:	$\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
	Fetch operands:	$\text{data1} \leftarrow \text{Reg}(\text{Rs}), \text{data2} \leftarrow \text{Reg}(\text{Rt})$
	Execute operation:	$\text{ALU_result} \leftarrow \text{func}(\text{data1}, \text{data2})$
	Write ALU result:	$\text{Reg}(\text{Rd}) \leftarrow \text{ALU_result}$
	Next PC address:	$\text{PC} \leftarrow \text{PC} + 4$
❖ I-type	Fetch instruction:	$\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
	Fetch operands:	$\text{data1} \leftarrow \text{Reg}(\text{Rs}), \text{data2} \leftarrow \text{Extend}(\text{imm16})$
	Execute operation:	$\text{ALU_result} \leftarrow \text{op}(\text{data1}, \text{data2})$
	Write ALU result:	$\text{Reg}(\text{Rt}) \leftarrow \text{ALU_result}$
	Next PC address:	$\text{PC} \leftarrow \text{PC} + 4$
❖ BEQ	Fetch instruction:	$\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
	Fetch operands:	$\text{data1} \leftarrow \text{Reg}(\text{Rs}), \text{data2} \leftarrow \text{Reg}(\text{Rt})$
	Equality:	$\text{zero} \leftarrow \text{subtract}(\text{data1}, \text{data2})$
	Branch:	if (zero) $\text{PC} \leftarrow \text{PC} + 4 + 4 \times \text{sign_ext}(\text{imm16})$ else $\text{PC} \leftarrow \text{PC} + 4$

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 9

Instruction Execution - cont'd

❖ LW	Fetch instruction:	$\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
	Fetch base register:	$\text{base} \leftarrow \text{Reg}(\text{Rs})$
	Calculate address:	$\text{address} \leftarrow \text{base} + \text{sign_extend}(\text{imm16})$
	Read memory:	$\text{data} \leftarrow \text{MEM}[\text{address}]$
	Write register Rt:	$\text{Reg}(\text{Rt}) \leftarrow \text{data}$
	Next PC address:	$\text{PC} \leftarrow \text{PC} + 4$
❖ SW	Fetch instruction:	$\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
	Fetch registers:	$\text{base} \leftarrow \text{Reg}(\text{Rs}), \text{data} \leftarrow \text{Reg}(\text{Rt})$
	Calculate address:	$\text{address} \leftarrow \text{base} + \text{sign_extend}(\text{imm16})$
	Write memory:	$\text{MEM}[\text{address}] \leftarrow \text{data}$
	Next PC address:	$\text{PC} \leftarrow \text{PC} + 4$
❖ Jump	Fetch instruction:	$\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
	Target PC address:	$\text{target} \leftarrow \text{PC}[31:28], \text{Imm26}, '00'$
	Jump:	$\text{PC} \leftarrow \text{target}$

concatenation

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 10

Requirements of the Instruction Set

- ❖ Memory
 - ❖ **Instruction memory** where instructions are stored
 - ❖ **Data memory** where data is stored
- ❖ Registers
 - ❖ **32 × 32-bit general purpose registers**, R0 is always zero
 - ❖ Read source register Rs
 - ❖ Read source register Rt
 - ❖ Write destination register Rt or Rd
- ❖ Program counter **PC register** and **Adder** to increment PC
- ❖ Sign and Zero **extender** for immediate constant
- ❖ **ALU** for executing instructions


Next ...

- ❖ Designing a Processor: Step-by-Step
- ❖ **Datapath Components and Clocking**
- ❖ Assembling an Adequate Datapath
- ❖ Controlling the Execution of Instructions
- ❖ The Main Controller and ALU Controller
- ❖ Drawback of the single-cycle processor design

Components of the Datapath


❖ Combinational Elements

 - ❖ ALU, Adder
- ❖ Immediate extender
- ❖ Multiplexers



❖ Storage Elements

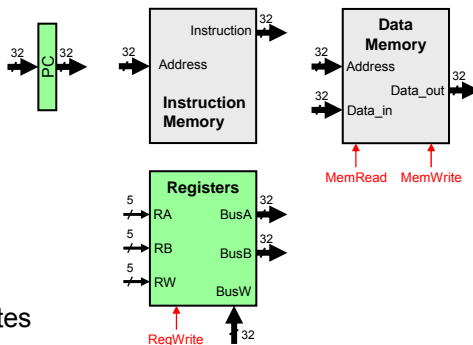- ❖ Instruction memory
- ❖ Data memory
- ❖ PC register
- ❖ Register file



❖ Clocking methodology


- ❖ Timing of reads and writes

Register Element

❖ Register

- ❖ Similar to the D-type Flip-Flop

❖ n-bit input and output

 

❖ Write Enable:


- ❖ Enable / disable writing of register
- ❖ Negated (0): Data_Out will not change
- ❖ Asserted (1): Data_Out will become Data_In **after clock edge**

❖ Edge triggered Clocking

- ❖ Register output is modified at **clock edge**

MIPS Register File

- ❖ Register File consists of 32×32 -bit registers
 - ❖ **BusA** and **BusB**: 32-bit output busses for reading 2 registers
 - ❖ **BusW**: 32-bit input bus for writing a register when **RegWrite** is 1
 - ❖ Two registers read and one written in a cycle
- ❖ Registers are selected by:
 - ❖ **RA** selects register to be read on **BusA**
 - ❖ **RB** selects register to be read on **BusB**
 - ❖ **RW** selects the register to be written
- ❖ Clock input
 - ❖ The clock input is **used ONLY** during write operation
 - ❖ During read, register file behaves as a **combinational logic** block
 - RA or RB valid => BusA or BusB valid after **access time**

 


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 15

Details of the Register File

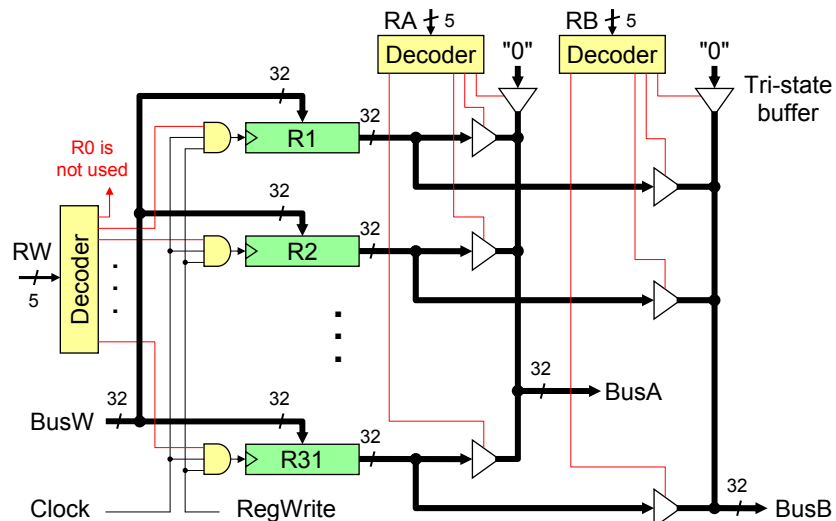



Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 16

Tri-State Buffers

  - ❖ Allow multiple sources to drive a single bus
- ❖ Two Inputs:
 - ❖ Data signal (data_in)
 - ❖ Output enable
- ❖ One Output (data_out):
 - ❖ If (Enable) Data_out = Data_in
 - else Data_out = High Impedance state (output is disconnected)
- ❖ Tri-state buffers can be used to build multiplexors




Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 17

Building a Multifunction ALU

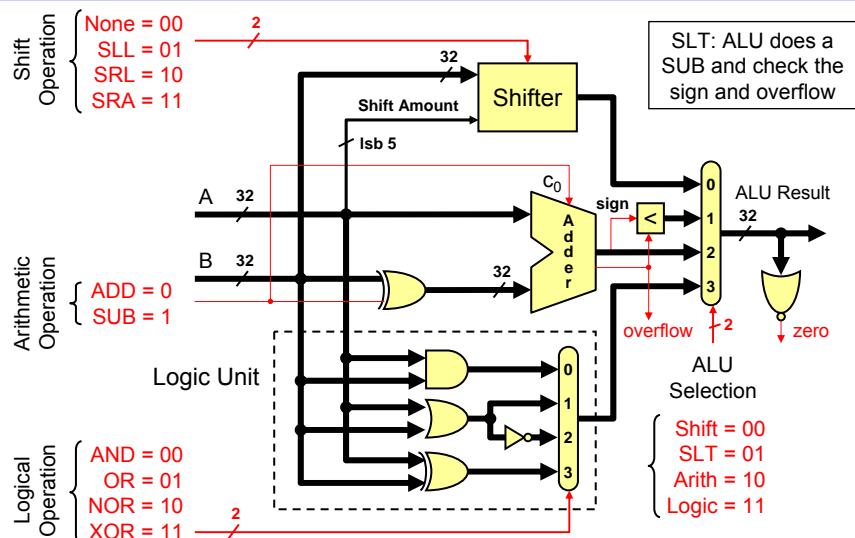


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 18

Instruction and Data Memories

- ❖ Instruction memory needs only provide read access
 - ❖ Because datapath does not write instructions
 - ❖ Behaves as combinational logic for read
 - ❖ **Address** selects **Instruction** after **access time**
- ❖ Data Memory is used for load and store
 - ❖ **MemRead**: enables output on **Data_out**
 - **Address** selects the word to put on **Data_out**
 - ❖ **MemWrite**: enables writing of **Data_in**
 - **Address** selects the memory word to be written
 - The **Clock** synchronizes the write operation
- ❖ Separate instruction and data memories
 - ❖ Later, we will replace them with **caches**

 


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 19

Clocking Methodology

- ❖ Clocks are needed in a sequential logic to decide when a state element (register) should be updated
- ❖ To ensure correctness, a **clocking methodology** defines when data can be written and read
- ❖ We assume **edge-triggered clocking**
- ❖ All state changes occur on the **same clock edge**
- ❖ Data must be **valid** and **stable** before arrival of clock edge
- ❖ Edge-triggered clocking allows a register to be read and written during same clock cycle

 


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 20

Determining the Clock Cycle

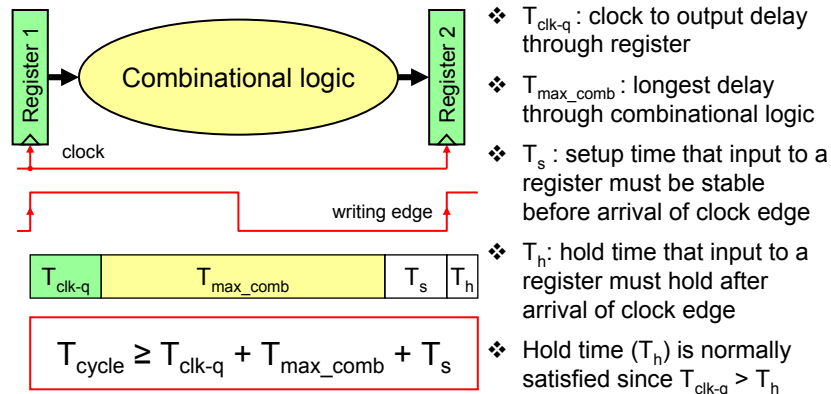- ❖ With edge-triggered clocking, the clock cycle must be long enough to accommodate the path from one register through the combinational logic to another register



Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 21

Clock Skew

- ❖ **Clock skew** arises because the clock signal uses **different paths** with slightly **different delays** to reach state elements
- ❖ Clock skew is the **difference in absolute time** between when two storage elements see a clock edge
- ❖ With a clock skew, the clock cycle time is increased

$$T_{\text{cycle}} \geq T_{\text{clk-q}} + T_{\text{max_combinational}} + T_{\text{setup}} + T_{\text{skew}}$$

- ❖ Clock skew is reduced by balancing the clock delays

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 22

Next ...

- ❖ Designing a Processor: Step-by-Step
- ❖ Datapath Components and Clocking
- ❖ **Assembling an Adequate Datapath**
- ❖ **Controlling the Execution of Instructions**
- ❖ The Main Controller and ALU Controller
- ❖ Drawback of the single-cycle processor design


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 23

Instruction Fetching Datapath

 - ❖ We can now assemble the datapath from its components
- ❖ For instruction fetching, we need ...
 - ❖ Program Counter (PC) register
 - ❖ Instruction Memory
 - ❖ Adder for incrementing PC




Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 24


Datapath for R-type Instructions

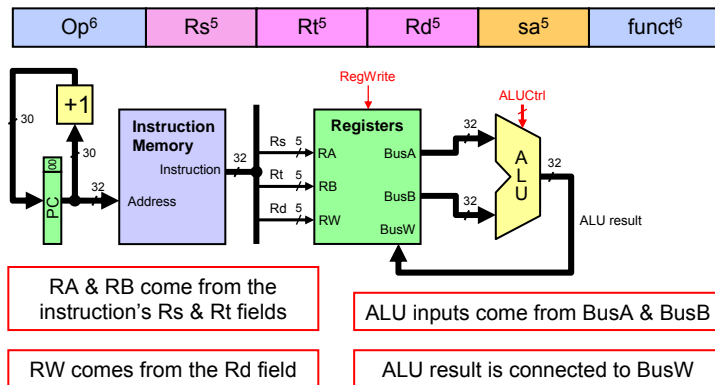

❖ Control signals

- ❖ ALU Ctrl is derived from the funct field because Op = 0 for R-type
- ❖ RegWrite is used to enable the writing of the ALU result


Datapath for I-type ALU Instructions

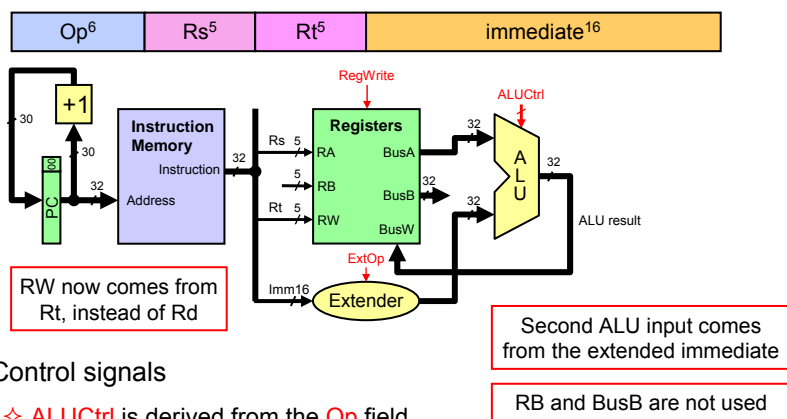

❖ Control signals

- ❖ ALU Ctrl is derived from the Op field
- ❖ RegWrite is used to enable the writing of the ALU result
- ❖ ExtOp is used to control the extension of the 16-bit immediate

Combining R-type & I-type Datapaths

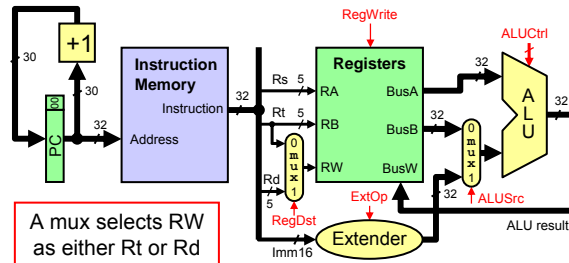

❖ Control signals



- ❖ ALU_{Ctrl} is derived from either the **Op** or the **funct** field
- ❖ **RegWrite** enables the writing of the **ALU result**
- ❖ **ExtOp** controls the extension of the 16-bit immediate
- ❖ **RegDst** selects the register destination as either **Rt** or **Rd**
- ❖ **ALUSrc** selects the 2nd ALU source as **BusB** or **extended immediate**

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 27

Controlling ALU Instructions

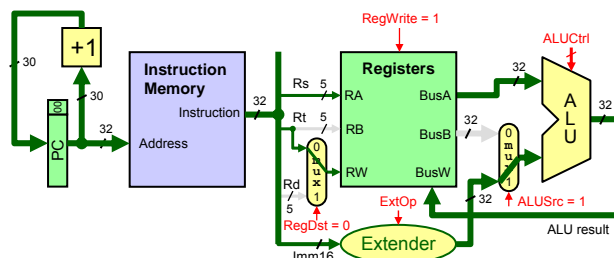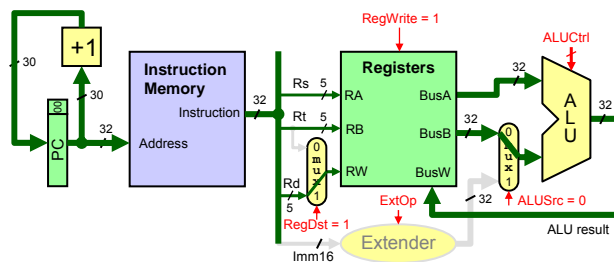


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 28

Details of the Extender

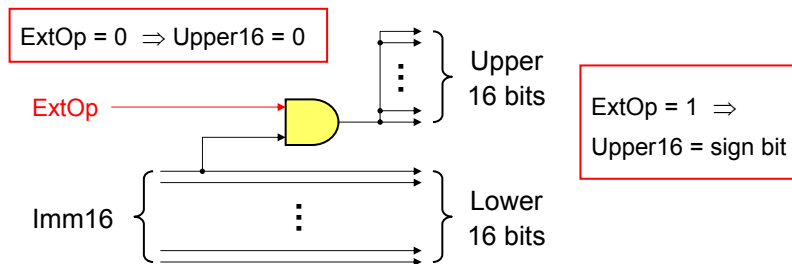- ❖ Two types of extensions
 - ❖ Zero-extension for unsigned constants
 - ❖ Sign-extension for signed constants
- ❖ Control signal **ExtOp** indicates type of extension
- ❖ Extender Implementation: wiring and one AND gate




Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 29

Adding Data Memory to Datapath

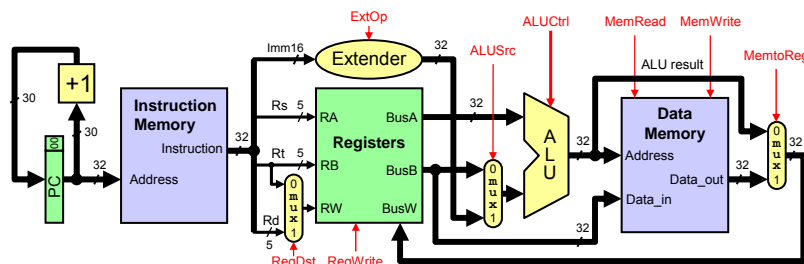- ❖ A **data memory** is added for **load** and **store** instructions



ALU calculates data memory address

A 3rd mux selects data on BusW as either ALU result or memory data_out

- ❖ Additional Control signals
 - ❖ **MemRead** for load instructions
 - ❖ **MemWrite** for store instructions
 - ❖ **MemtoReg** selects data on BusW as **ALU result** or **Memory Data_out**


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 30

Controlling the Execution of Load

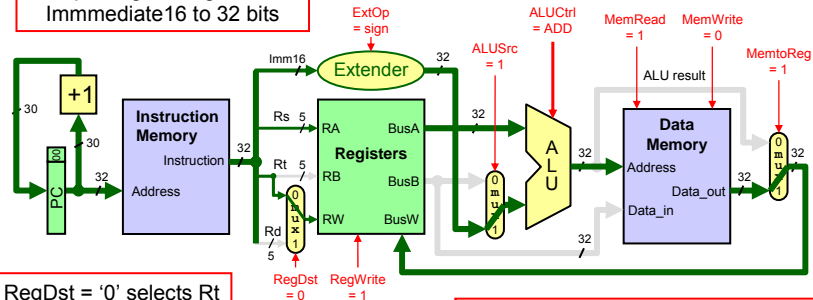ExtOp = 'sign' to sign-extend Immediate16 to 32 bits



RegDst = '0' selects Rt as destination register

MemRead = '1' to read data memory

ALUSrc = '1' selects extended immediate as second ALU input


MemtoReg = '1' places the data read from memory on BusW

ALUctrl = 'ADD' to calculate data memory address as $\text{Reg}(Rs) + \text{sign-extend}(\text{Imm16})$

RegWrite = '1' to write the memory data on BusW to register Rt

Controlling the Execution of Store

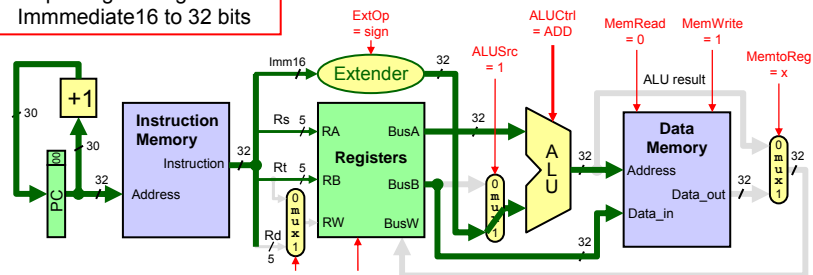ExtOp = 'sign' to sign-extend Immediate16 to 32 bits



RegDst = 'x' because no destination register

MemWrite = '1' to write data memory


ALUSrc = '1' to select the extended immediate as second ALU input

MemtoReg = 'x' because we don't care what data is placed on BusW

ALUctrl = 'ADD' to calculate data memory address as $\text{Reg}(Rs) + \text{sign-extend}(\text{Imm16})$

RegWrite = '0' because no register is written by the store instruction

Adding Jump and Branch to Datapath

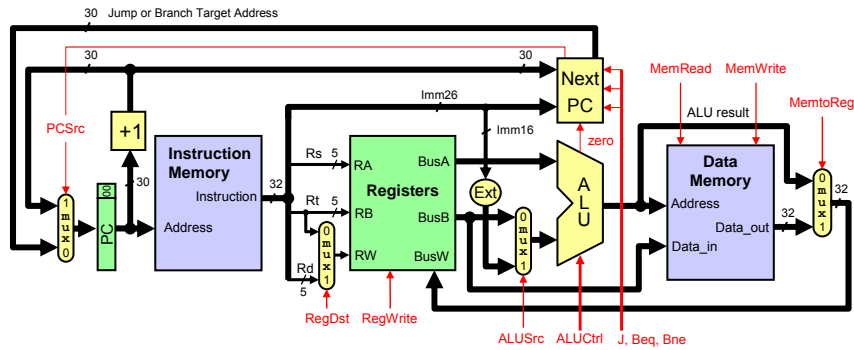


❖ Additional Control Signals

- ❖ **J, Beq, Bne** for jump and branch instructions
- ❖ **Zero** condition of the ALU is examined
- ❖ **PCSrc = 1** for Jump & taken Branch

Next PC computes jump or branch target instruction address

For Branch, ALU does a subtraction

Details of Next PC

 


Imm16 is sign-extended to 30 bits

Jump target address: upper 4 bits of PC are concatenated with Imm26

$$PCSrc = J + (Beq \cdot Zero) + (Bne \cdot \overline{Zero})$$

Controlling the Execution of Jump

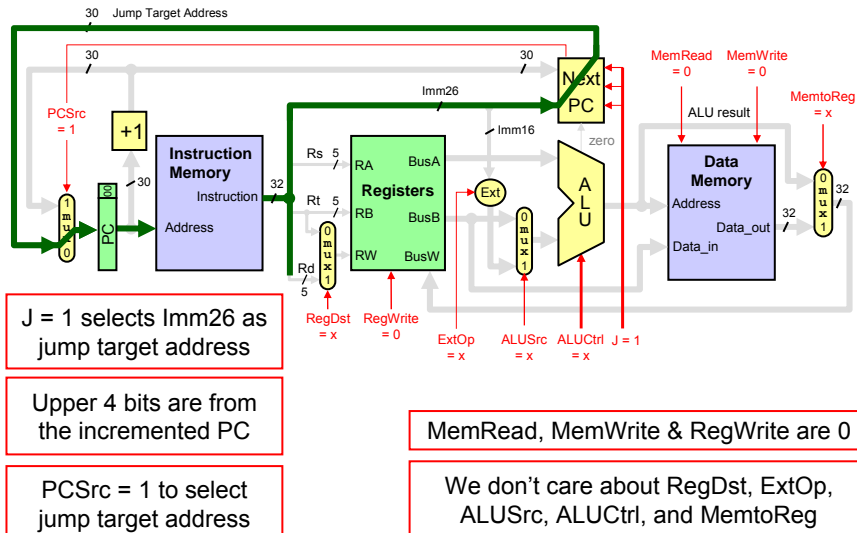


Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 35

Controlling the Execution of Branch

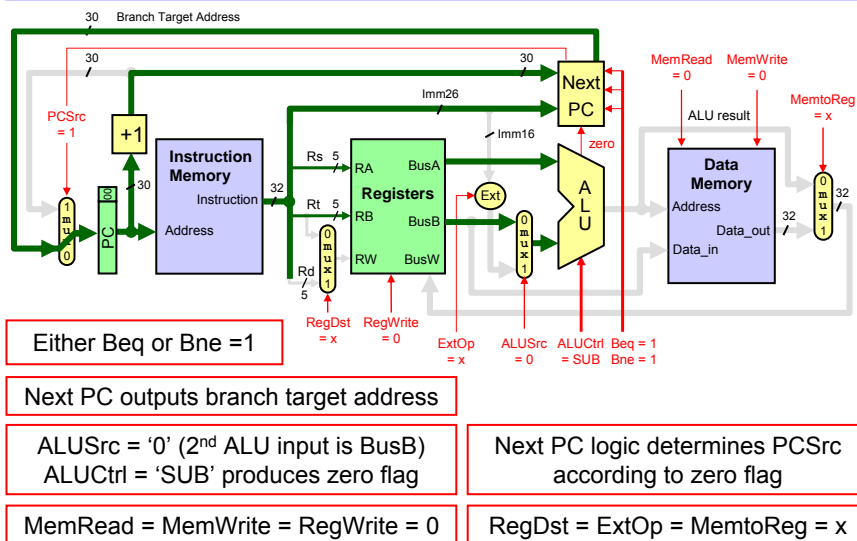

Single Cycle Processor Design


COE 308 – Computer Architecture

© Muhamed Mudawar – slide 36


Next ...

- ❖ Designing a Processor: Step-by-Step
- ❖ Datapath Components and Clocking
- ❖ Assembling an Adequate Datapath
- ❖ Controlling the Execution of Instructions
- ❖ **The Main Controller and ALU Controller**
- ❖ Drawback of the single-cycle processor design

Main Control and ALU Control

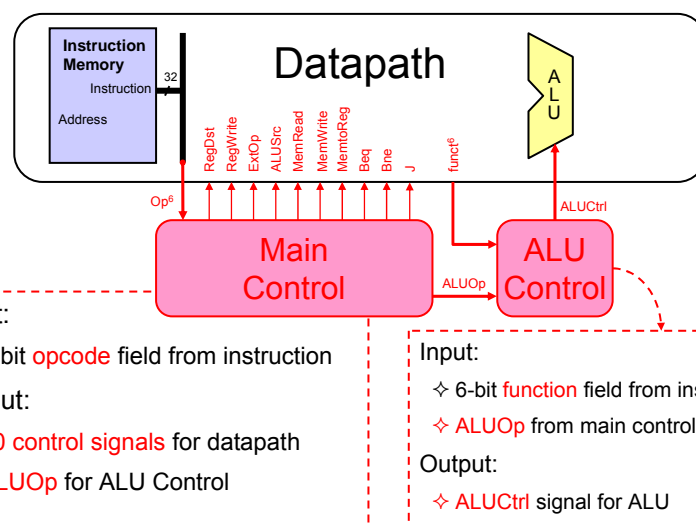

Single-Cycle Datapath + Control

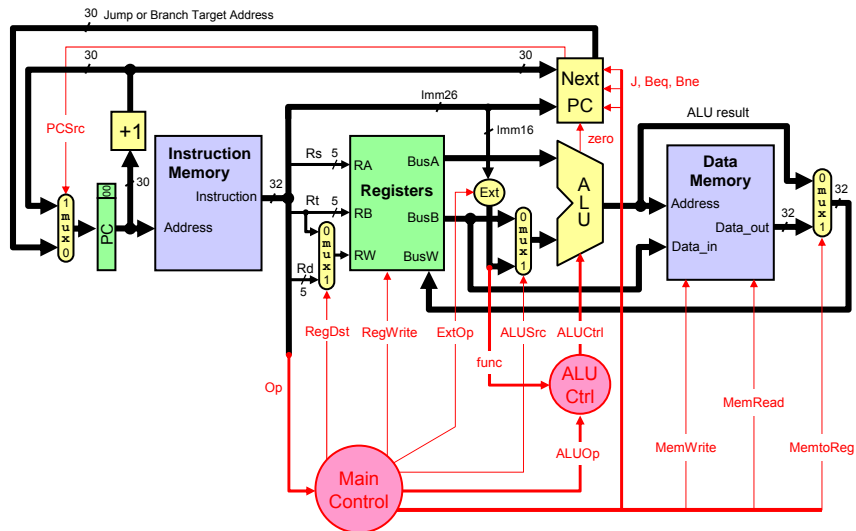

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 39

Main Control Signals

Signal	Effect when '0'	Effect when '1'
RegDst	Destination register = Rt	Destination register = Rd
RegWrite	None	Destination register is written with the data value on BusW
ExtOp	16-bit immediate is zero-extended	16-bit immediate is sign-extended
ALUSrc	Second ALU operand comes from the second register file output (BusB)	Second ALU operand comes from the extended 16-bit immediate
MemRead	None	Data memory is read Data_out ← Memory[address]
MemWrite	None	Data memory is written Memory[address] ← Data_in
MemtoReg	BusW = ALU result	BusW = Data_out from Memory
Beq, Bne	PC ← PC + 4	PC ← Branch target address If branch is taken
J	PC ← PC + 4	PC ← Jump target address
ALUOp	This multi-bit signal specifies the ALU operation as a function of the opcode	

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 40

Main Control Signal Values

Op	Reg Dst	Reg Write	Ext Op	ALU Src	ALU Op	Beq	Bne	J	Mem Read	Mem Write	Mem toReg
R-type	1 = Rd	1	x	0=BusB	R-type	0	0	0	0	0	0
addi	0 = Rt	1	1=sign	1=Imm	ADD	0	0	0	0	0	0
slli	0 = Rt	1	1=sign	1=Imm	SLT	0	0	0	0	0	0
andi	0 = Rt	1	0=zero	1=Imm	AND	0	0	0	0	0	0
ori	0 = Rt	1	0=zero	1=Imm	OR	0	0	0	0	0	0
xori	0 = Rt	1	0=zero	1=Imm	XOR	0	0	0	0	0	0
lw	0 = Rt	1	1=sign	1=Imm	ADD	0	0	0	1	0	1
sw	x	0	1=sign	1=Imm	ADD	0	0	0	0	1	x
beq	x	0	x	0=BusB	SUB	1	0	0	0	0	x
bne	x	0	x	0=BusB	SUB	0	1	0	0	0	x
j	x	0	x	x	x	0	0	1	0	0	x

❖ X is a don't care (can be 0 or 1), used to minimize logic

Logic Equations for Control Signals

$$\text{RegDst} \leq \text{R-type}$$

$$\text{RegWrite} \leq (\text{sw} + \text{beq} + \text{bne} + \text{j})$$


$$\text{ExtOp} \leq (\text{andi} + \text{ori} + \text{xori})$$

$$\text{ALUSrc} \leq (\text{R-type} + \text{beq} + \text{bne})$$

$$\text{MemRead} \leq \text{lw}$$

$$\text{MemWrite} \leq \text{sw}$$

$$\text{MemtoReg} \leq \text{lw}$$

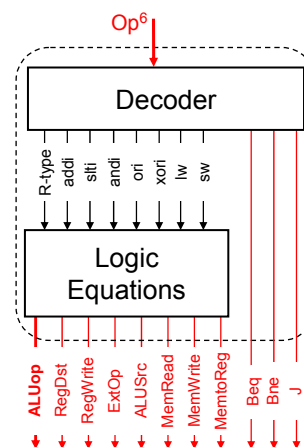

ALU Control Truth Table

Op ⁶	ALU Control			4-bit Encoding
	ALUOp	funct ⁶	ALUCtrl	
R-type	R-type	add	ADD	0000
R-type	R-type	sub	SUB	0010
R-type	R-type	and	AND	0100
R-type	R-type	or	OR	0101
R-type	R-type	xor	XOR	0110
R-type	R-type	slt	SLT	1010
addi	ADD	x	ADD	0000
slli	SLT	x	SLT	1010
andi	AND	x	AND	0100
ori	OR	x	OR	0101
xori	XOR	x	XOR	0110
lw	ADD	x	ADD	0000
sw	ADD	x	ADD	0000
beq	SUB	x	SUB	0010
bne	SUB	x	SUB	0010
j	x	x	x	x

The 4-bit encoding for ALUctrl is chosen here to be equal to the last 4 bits of the function field

Other binary encodings are also possible. The idea is to choose a binary encoding that will minimize the logic for ALU Control

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 43

Next ...

- ❖ Designing a Processor: Step-by-Step
- ❖ Datapath Components and Clocking
- ❖ Assembling an Adequate Datapath
- ❖ Controlling the Execution of Instructions
- ❖ The Main Controller and ALU Controller
- ❖ Drawback of the single-cycle processor design

Single Cycle Processor Design


COE 308 – Computer Architecture

© Muhamed Mudawar – slide 44

Drawbacks of Single Cycle Processor

❖ Long cycle time

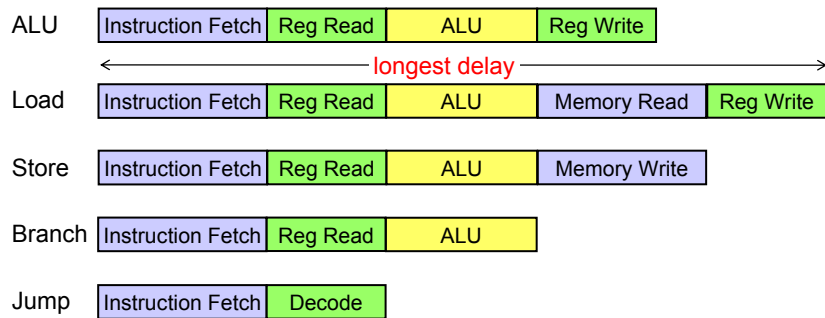- ❖ All instructions take as much time as the **slowest**



❖ Alternative Solution: **Multicycle** implementation

- ❖ Break down instruction execution into multiple cycles

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 45

Multicycle Implementation

❖ Break instruction execution into **five steps**

- ❖ Instruction fetch
- ❖ Instruction decode and register read
- ❖ Execution, memory address calculation, or branch completion
- ❖ Memory access or ALU instruction completion
- ❖ Load instruction completion

❖ **One step = One clock cycle** (clock cycle is reduced)

- ❖ First 2 steps are the same for all instructions

Instruction	# cycles	Instruction	# cycles
ALU & Store	4	Branch	3
Load	5	Jump	2

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 46

Performance Example

- ❖ Assume the following operation times for components:
 - ❖ Instruction and data memories: 200 ps
 - ❖ ALU and adders: 180 ps
 - ❖ Decode and Register file access (read or write): 150 ps
 - ❖ Ignore the delays in PC, mux, extender, and wires
- ❖ Which of the following would be faster and by how much?
 - ❖ Single-cycle implementation for all instructions
 - ❖ Multicycle implementation optimized for every class of instructions
- ❖ Assume the following instruction mix:
 - ❖ 40% ALU, 20% Loads, 10% stores, 20% branches, & 10% jumps

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 47

Solution

Instruction Class	Instruction Memory	Register Read	ALU Operation	Data Memory	Register Write	Total
ALU	200	150	180		150	680 ps
Load	200	150	180	200	150	880 ps
Store	200	150	180	200		730 ps
Branch	200	150	180			530 ps
Jump	200	150	← decode and update PC			300 ps


- ❖ For fixed single-cycle implementation:
 - ❖ Clock cycle = 880 ps determined by longest delay (load instruction)
- ❖ For multi-cycle implementation:
 - ❖ Clock cycle = $\max(200, 150, 180) = 200$ ps (maximum delay at any step)
 - ❖ Average CPI = $0.4 \times 4 + 0.2 \times 5 + 0.1 \times 4 + 0.2 \times 3 + 0.1 \times 2 = 3.8$
- ❖ Speedup = $880 \text{ ps} / (3.8 \times 200 \text{ ps}) = 880 / 760 = 1.16$

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 48

Worst Case Timing (Load Instruction)

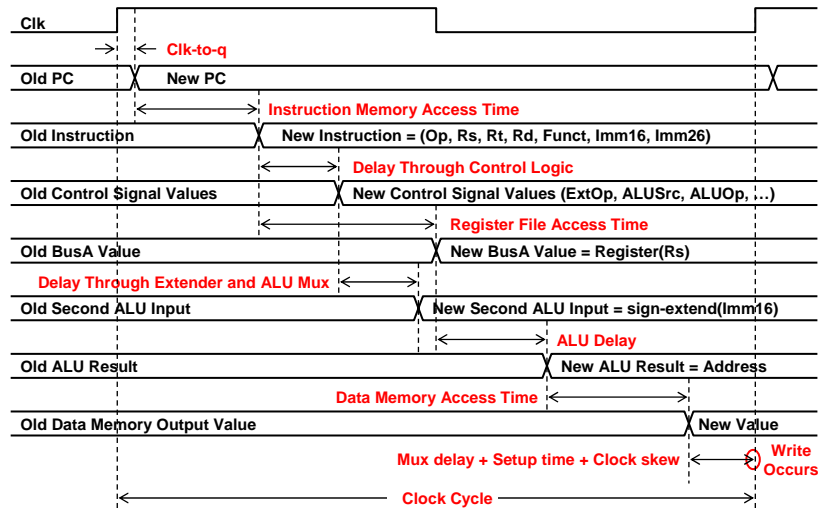

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 49

Worst Case Timing - Cont'd

- ❖ Long cycle time: must be long enough for **Load** operation
 - PC's Clk-to-Q
 - + Instruction Memory's Access Time
 - + Maximum of (
 - Register File's Access Time,
 - Delay through control logic + extender + ALU mux)
 - + ALU to Perform a 32-bit Add
 - + Data Memory Access Time
 - + Delay through MemtoReg Mux
 - + Setup Time for Register File Write + Clock Skew
- ❖ Cycle time is **longer than needed** for other instructions
 - ✧ Therefore, single cycle processor design is not used in practice

Single Cycle Processor Design

COE 308 – Computer Architecture

© Muhamed Mudawar – slide 50

Summary

- ❖ 5 steps to design a processor
 - ✧ Analyze instruction set => **datapath requirements**
 - ✧ Select **datapath components** & establish **clocking methodology**
 - ✧ **Assemble datapath** meeting the requirements
 - ✧ Analyze **implementation of each instruction** to determine **control signals**
 - ✧ Assemble the **control logic**
- ❖ MIPS makes Control easier
 - ✧ Instructions are of same size
 - ✧ Source registers always in same place
 - ✧ Immediates are of same size and same location
 - ✧ Operations are always on registers/immediates
- ❖ Single cycle datapath => CPI=1, but Long Clock Cycle