


 



| | | | | | | יפי | nals - | con | <u> </u> | |
|--------|------------------|----------------------------------|--------|-----|-----|-----|---------------------------------|----------|----------|---------------------|
| Ор | Decode Signal | Execute Stage Control Signals | | | | | Memory Stage Control Signals | | | Writeback Signal |
| | RegDst | ALUSrc | ALUOp | Beq | Bne | j | MemRead | MemWrite | MemtoReg | RegWrite |
| R-Type | 1=Rd | 0=Reg | R-Type | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| addi | 0=Rt | 1=lmm | ADD | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| slti | 0=Rt | 1=lmm | SLT | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| andi | 0=Rt | 1=lmm | AND | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| ori | 0=Rt | 1=lmm | OR | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| lw | 0=Rt | 1=lmm | ADD | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| SW | x | 1=lmm | ADD | 0 | 0 | 0 | 0 | 1 | x | 0 |
| beq | x | 0=Reg | SUB | 1 | 0 | 0 | 0 | 0 | x | 0 |
| bne | x | 0=Reg | SUB | 0 | 1 | 0 | 0 | 0 | x | 0 |
| i | x | x | х | 0 | 0 | 1 | 0 | 0 | х | 0 |

 


 


 





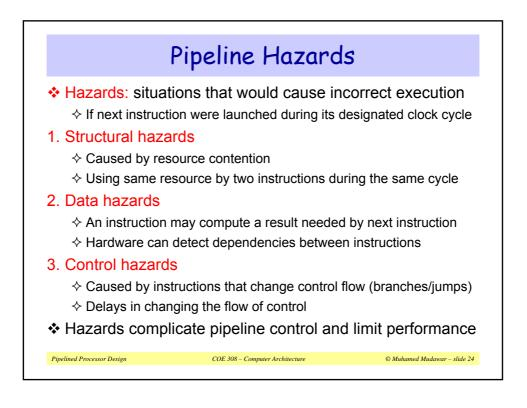


 


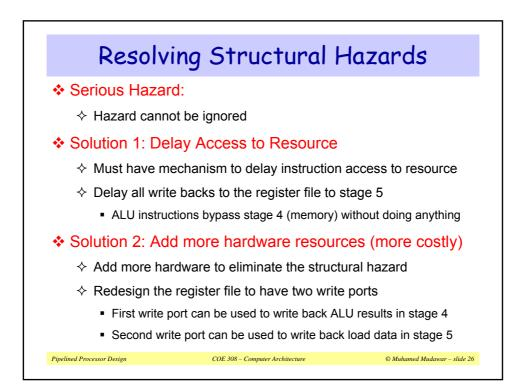


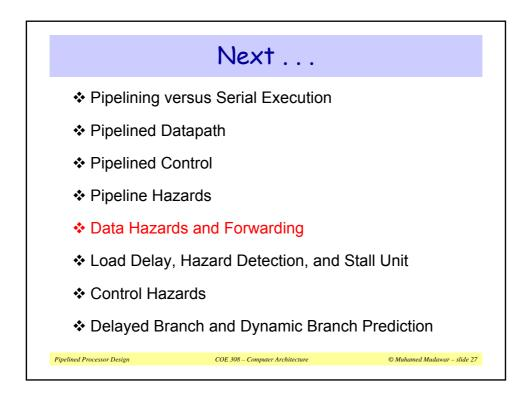


 


 


 

 


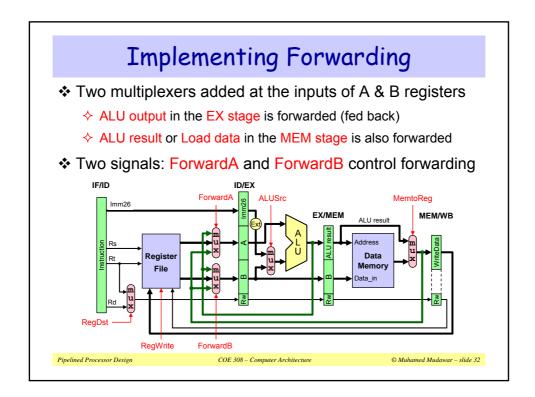


 


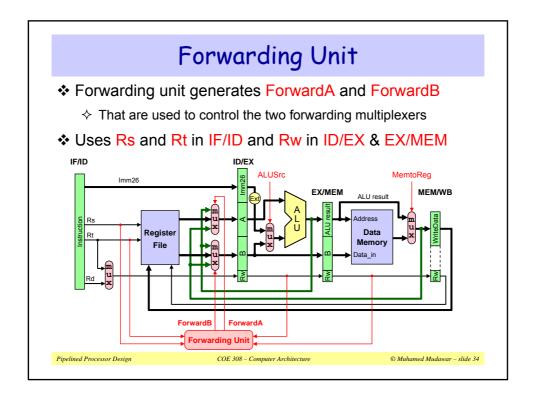



| Forwarding Control Signals | | | | | | |
|----------------------------|---|--|--|--|--|--|
| Control Signal | Explanation | | | | | |
| ForwardA = 00 | First ALU operand comes from the register file | | | | | |
| ForwardA = 01 | Forwarded from the previous ALU result | | | | | |
| ForwardA = 10 | Forwarded from data memory or 2 nd previous ALU result | | | | | |
| ForwardB = 00 | Second ALU operand comes from the register file | | | | | |
| ForwardB = 01 | Forwarded from the previous ALU result | | | | | |
| ForwardB = 10 | Forwarded from data memory or 2 nd previous ALU result | | | | | |
| if (IF/ID.Rs = | == ID/EX.Rw≠0 and ID/EX.RegWrite) ForwardA = 0 | | | | | |
| elseif (IF/ID.Rs = | == EX/MEM.Rw ≠ 0 and EX/MEM.RegWrite) ForwardA = 10 | | | | | |
| else ForwardA = | : 00 | | | | | |
| if (IF/ID.Rt = | == ID/EX.Rw≠0 and ID/EX.RegWrite) ForwardB = 01 | | | | | |
| elseif (IF/ID.Rt = | = EX/MEM.Rw≠0 and EX/MEM.RegWrite) ForwardB = 10 | | | | | |
| else ForwardB = | 00 | | | | | |
| Pipelined Processor Design | COE 308 – Computer Architecture © Muhamed Mudawar – slide 35 | | | | | |

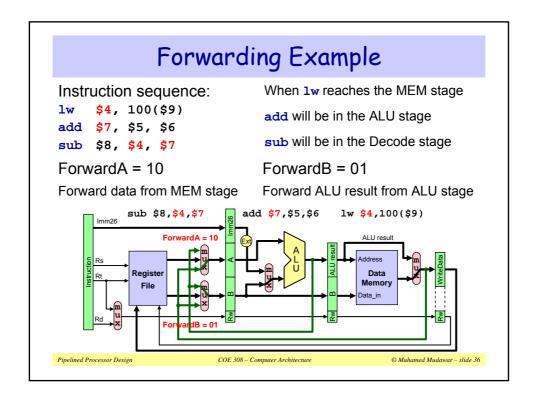


 

 

 

 

 

| | Comp | iler Schedu | lling | 9 | | |
|---------------------------|-------------------------------|---------------------------------|--------|-------------------------------|--|--|
| Compi | lers can scheo | dule code in a way | y to a | void load stalls | | |
| ✤ Consid | ler the followir | ng statements: | | | | |
| a = b |) + c; d = e - f; | | | | | |
| Slow c | ode: | Fast code: No Stalls | | | | |
| lw | \$10, (\$1) | # \$1 = addr b | lw | \$10, 0(\$1) | | |
| lw | <mark>\$11</mark> , (\$2) | # \$2 = addr c | lw | <mark>\$11</mark> , 0(\$2) | | |
| add | \$12, \$10, <mark>\$11</mark> | # stall | lw | \$13, 0(\$4) | | |
| SW | \$12, (\$3) | #\$3 = addr a | lw | <mark>\$14</mark> , 0(\$5) | | |
| lw | \$13, (\$4) | #\$4 = addr e | add | \$12, \$10, <mark>\$11</mark> | | |
| lw | <mark>\$14</mark> , (\$5) | # \$5 = addr f 🦯 | SW | \$12, 0(\$3) | | |
| sub | \$15, \$13, <mark>\$14</mark> | # stall | sub | \$15, \$13, <mark>\$14</mark> | | |
| SW | \$15, (\$6) | # \$6 = addr d | SW | \$14, 0(\$6) | | |
| Pipelined Processor D | esign | COE 308 – Computer Architecture | | © Muhamed Mudawar – slide 42 | | |

